

**II B. Tech I Semester Regular Examinations, March - 2021**  
**ELECTRICAL CIRCUIT ANALYSIS**  
**(Electrical and Electronics Engineering)**

Time: 3 Hours

Max. Marks: 60

**Note:** Answer **ONE** question from each unit ( $5 \times 12 = 60$  Marks)

~~~~~  
**UNIT-I**

1. a) A balanced Y-connected load with a phase impedance of  $40+j25\Omega$  is supplied [6M]  
by a balanced, positive sequence  $\Delta$  - connected source with a line voltage of 210 V. Calculate the phase currents? Use  $V_{RY}$  as reference.

- b) Briefly explain about three phase balanced star system. [6M]

**(OR)**

2. a) A unbalanced  $\Delta$  - connected load having phase impedances  $Z_{RY} = 3+j4\Omega$ , [6M]  
 $Z_{YB} = 4+j5\Omega$  and  $Z_{BR} = 6+j8\Omega$  connected to a balanced  $\Delta$  - source of line voltage 420V. Then calculate


i) Phase voltages      ii) Phase currents      iii) Line currents

- b) Obtain the relationship between line voltage and phase voltages in star [6M]  
connected system with necessary diagrams.

**UNIT-II**

3. a) Derive an expression for DC transient current in RL series circuit. [6M]

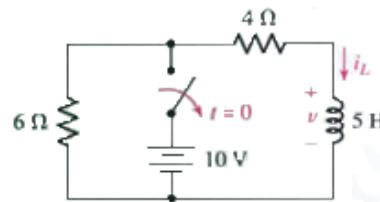- b) Find the inductor voltage for the following circuit. [6M]




**(OR)**

4. a) In a series RL circuit,  $R = 8$  ohms,  $L = 4H$ . A DC voltage of 100 V is applied [6M]  
at  $t = 0$ . Obtain the expression for  $i(t)$  and  $V_L(t)$ .

- b) Derive an expression for DC transient current in RC series circuit and what is [6M]  
the need of Laplace transforms in transient analysis.

**UNIT-III**

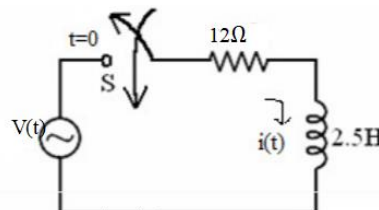
5. a) A sinusoidal voltage of  $120\sin 50t$  is applied to a series circuit of  $R = 12\Omega$  and [6M]  
 $L = 2.5H$  at  $t = 0$  shown in below Figure. By Laplace transform method,  
determine the current  $i(t)$  for all  $t \geq 0$ . Assume zero initial conditions.



- b) Derive the expression for transient response in series R-L circuit for AC [6M]  
excitation. Obtain the solution using Laplace transforms.


(OR)

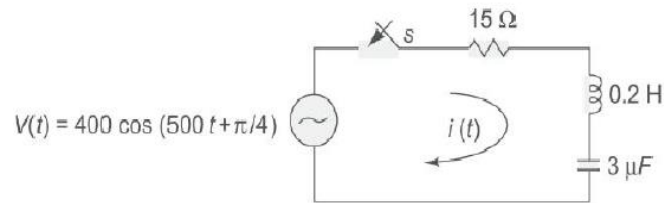6. a) Derive the expression for transient response in series R-L-C circuit for AC [6M]  
excitation. Obtain the solution using Laplace transforms.
- b) In the circuit shown in Figure, determine the complete solution for the current, [6M]  
when the switch is closed at  $t = 0$ .



**UNIT-IV**

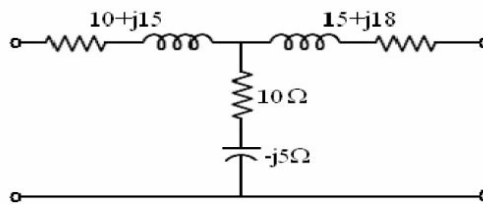
7. a) For the two-port network shown below, determine Z parameters. [6M]



- b) With suitable examples explain about cascaded networks. [6M]

(OR)

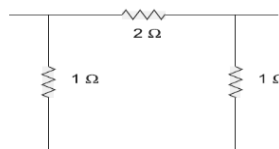8. a) Determine the transmission parameters for the network shown in Figure. [6M]



- b) For a simple two port network derive Y- parameters and why these are called [6M]  
short circuit parameters?

**UNIT-V**

9. a) Explain Cauer method to synthesize driving point LC immittance function. [6M]
- b) The driving point Impedance function of a network is given by [6M]  
 $Z(S) = S(S^2+10) / ((S^2+4)(S^2+16))$ . Realize the network in first Foster form.

(OR)

10. a) Explain in brief about network synthesis. [6M]
- b) Explain the Foster and Cauer forms of RC networks. [6M]

\*\*\*\*\*