

III B. TECH I SEMESTER REGULAR EXAMINATIONS, NOVEMBER - 2022
ELECTRICAL MEASUREMENTS AND INSTRUMENTATION
(Electrical and Electronics Engineering)

Time: 3 Hours

Max. Marks: 70

Note: Answer ONE question from each unit (5 × 14 = 70 Marks)

~~~~~

UNIT-I

1. a) Identify the type of torque is responsible for operation of measuring instrument-Justify your answer with proper reason? [7M]
- b) How the extension of ammeter is possible? Analyze with proper circuit diagram. [7M]

(OR)

2. a) What does meant by current transformer – mention its importance by the help of applications. [7M]
- b) A meter reads 127.50V and the true value of voltage is 127.43. Obtain the [7M]  
i) the static error    ii) the static correction for this instrument.

UNIT-II

3. a) Dynamometer wattmeter used for measurement of power – Interpret your answer for 3-Phase power measurement of unbalanced load. [7M]
- b) A wattmeter has a current coil of 0.1  $\Omega$  resistances and pressure coil of 6500  $\Omega$  resistance. Calculate the percentage errors, due to resistance only with each of the methods of connection, when reading the input to an apparatus which takes: [7M]  
(i) 12 A at 250 V with unity power power factor, and  
(ii) 12 A at 250 V and 0.4 power factor

(OR)


4. a) By the help of neat diagram, write about the power factor meter in detail? [7M]
- b) Weston type synchroscope is used for condition of synchronization – explore your justification regarding to this statement? [7M]

UNIT-III

5. a) Explain the term “standardization” of potentiometer. Describe the procedure of standardization of DC potentiometer with neat diagram. [7M]
- b) Write about Wheat stone’s bridge operation for measurement of medium resistances with necessary balance expression? [7M]

(OR)

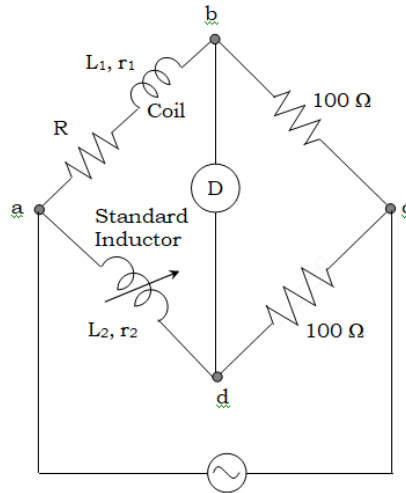6. a) Illustrate the Maxwell's Inductance Bridge operation by [7M]  
representing the phasor diagram.
- b) A Maxwell's inductance comparison bridge is shown in Figure. [7M]  
Arm ab consists of a coil with inductance  $L_1$  and resistance  $r_1$  in series with a non-inductive resistance  $R$ . Arm bc and ad are each a non-inductive resistance of  $100 \Omega$ . Arm cd consists of standard variable inductor  $L_2$  of resistance  $32.7 \Omega$ . Balance is obtained when  $L_2 = 47.8 \text{ mH}$  and  $R = 1.36 \Omega$ . Find the resistance and inductance of coil in arm ab.



## UNIT-IV

7. a) Describe the different electrical methods for measurement of [7M]  
liquid level using transducer.
- b) Write about the operation of Piezo electric and Photo Diode [7M]  
Transducers?

(OR)

8. a) How the Pressure can be determined using transducer – Justify [7M]  
your answer with neat diagram by any one method.
- b) With suitable method, outline the measurement of Angular [7M]  
velocity and its operation?

## UNIT-V

9. a) In view of following parameters, summarize the digital meters [7M]  
advantages. i) Accuracy ii) Resolution iii) Power requirements  
iv) Cost and Portability
- b) Illustrate the basic block diagram of digital voltmeter and [7M]  
present its operation.

(OR)

10. a) Write about digital frequency working with necessary diagram. [7M]
- b) Explain the working of digital multimeter with block diagram. [7M]

\* \* \* \* \*